

week2_circuits_form

Saturday, May 30, 2020 12:43 PM

Problem 1: Calculate the following values:

The total resistance in the circuit, R_t

$$2.875 \times 10^3 \Omega \text{ or } 2.875 \text{ k}\Omega$$

Calculate the current through R_1

$$1.739 \times 10^{-3} \text{ amp.}$$

Calculate the current through R_2

$$6.522 \times 10^{-4} \text{ amp.}$$

Calculate the current through R_3

$$1.087 \times 10^{-3} \text{ amp.}$$

Calculate the voltage across R_1


$$1.739 \text{ volts.}$$

Calculate the voltage across R_2

$$3.261 \text{ volts.}$$

Calculate the voltage across R_3

$$3.261 \text{ volts.}$$

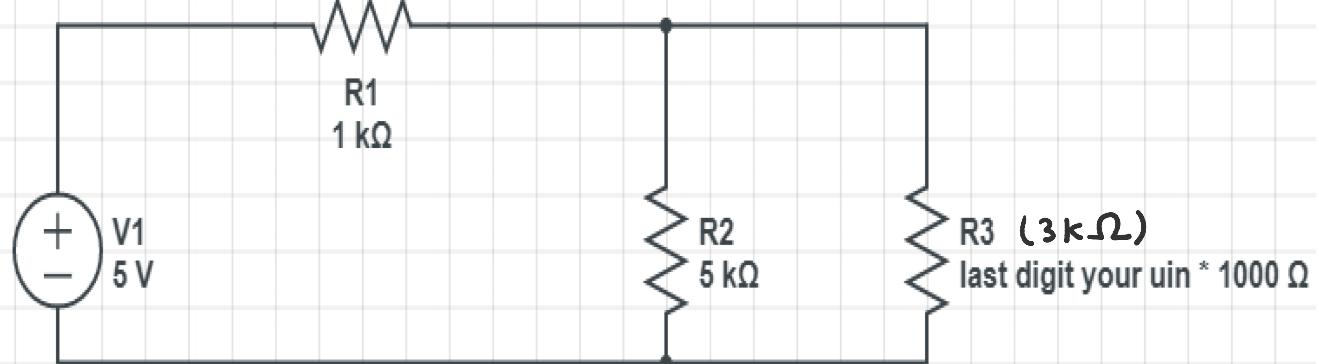

Circuit for Problem 1

Use this space to show your work for problem 1

$$R_T = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = 1 + \frac{1}{\frac{1}{5} + \frac{1}{3}} = 1 + \frac{15}{8} = 2.875 \text{ k}\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{5}{2.875 \times 10^3} = 1.739 \times 10^{-3} \text{ amp.}$$

so, $I_1 = 1.739 \times 10^{-3} \text{ amp}$

$$\Rightarrow V_1 = (1.739 \times 10^{-3})(1 \times 10^3) = 1.739 \text{ volt.}$$

$$V_2 = V_3 = V_T - V_1 = 5 - 1.739 = 3.261 \text{ volt.}$$

$$I_2 = \frac{3.261}{5 \times 10^3} = 0.6522 \times 10^{-3} \text{ amp}$$

$$I_3 = \frac{3.261}{3 \times 10^3} = 1.087 \times 10^{-3} \text{ amp.}$$

Problem 2: Calculate the following values:

The total resistance in the circuit, R_t

$$9.505 \text{ k}\Omega.$$

Calculate the current through R_1

$$2.025 \times 10^{-4} \text{ amp.}$$

Calculate the current through R_2

$$3.24 \times 10^{-4} \text{ amp.}$$

Calculate the current through R_3

$$5.26 \times 10^{-4} \text{ amp.}$$

Calculate the current through R_4

$$3.75 \times 10^{-4} \text{ amp.}$$

Calculate the current through R_5

$$1.5 \times 10^{-4} \text{ amp.}$$

Calculate the voltage across R_1


$$1.62 \text{ volts}$$

Calculate the voltage across R_2

$$1.62 \text{ volts}$$

Calculate the voltage across R_3

$$2.63 \text{ volts}$$

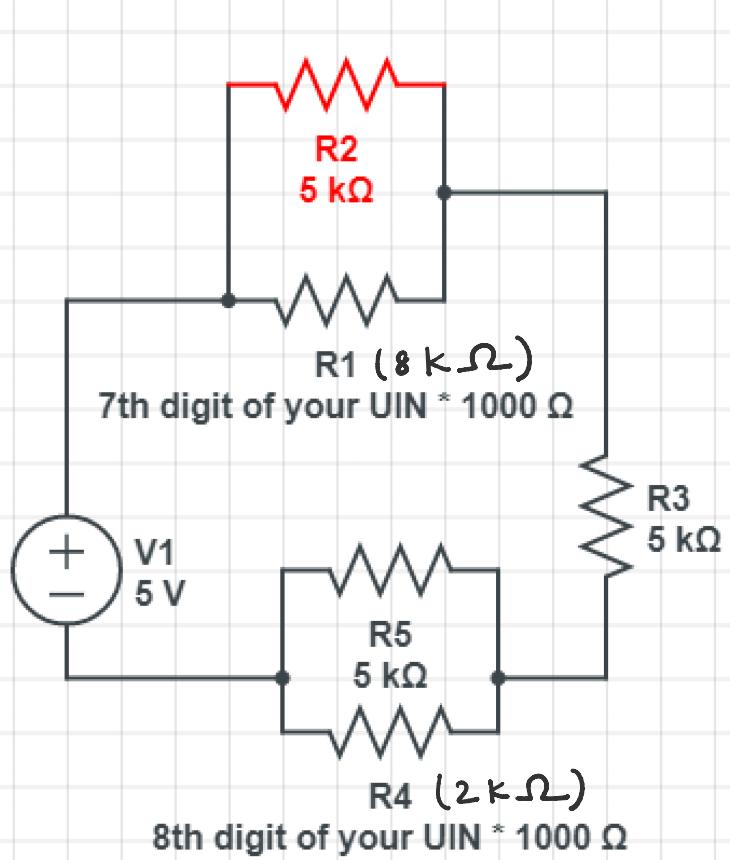

Circuit for Problem 2

Calculate the voltage across R_4

$$0.75 \text{ volts.}$$

Calculate the voltage across R_5

$$0.75 \text{ volts.}$$

Use this space to show your work for problem 2

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} + R_3 + \frac{1}{\frac{1}{R_4} + \frac{1}{R_5}} = \frac{1}{\frac{1}{8} + \frac{1}{5}} + 5 + \frac{1}{\frac{1}{2} + \frac{1}{5}} = \frac{40}{13} + 5 + \frac{10}{7} = 9.505 \text{ k}\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{5 \text{ volts}}{9.505 \text{ k}\Omega} = 5.26 \times 10^{-4} \text{ amp.}$$

$$\text{So, } I_3 = 5.26 \times 10^{-4} \text{ amp.}$$

$$V_3 = (5.26 \times 10^{-4})(5 \times 10^3) = 2.63 \text{ volts.}$$

$$R_{12} = \frac{1}{\frac{1}{8} + \frac{1}{5}} = \frac{40}{13} = 3.077 \text{ k}\Omega.$$

$$R_{45} = \frac{1}{\frac{1}{2} + \frac{1}{5}} = \frac{10}{7} = 1.430 \text{ k}\Omega.$$

$$I_{12} = I_{45} = I_T = 5.26 \times 10^{-4} \text{ amp.}$$

$$V_{12} = (I_{12})(R_{12}) = (5.26 \times 10^{-4})(3.077 \times 10^3) = 1.62 \text{ volts.}$$

$$V_{45} = (I_{45})(R_{45}) = (5.26 \times 10^{-4})(1.430 \times 10^3) = 0.75 \text{ volts.}$$

$$\text{So, } V_1 = V_2 = 1.62 \text{ volts.}$$

$$V_4 = V_5 = 0.75 \text{ volts.}$$


$$I_1 = \frac{V_1}{R_1} = \frac{1.62}{8 \times 10^3} = 2.025 \times 10^{-4} \text{ amp.}$$

$$I_2 = \frac{V_2}{R_2} = \frac{1.62}{5 \times 10^3} = 3.24 \times 10^{-4} \text{ amp.}$$

$$I_4 = \frac{V_4}{R_4} = \frac{0.75}{2 \times 10^3} = 3.75 \times 10^{-4} \text{ amp.}$$

$$I_5 = \frac{V_5}{R_5} = \frac{0.75}{5 \times 10^3} = 1.5 \times 10^{-4} \text{ amp.}$$

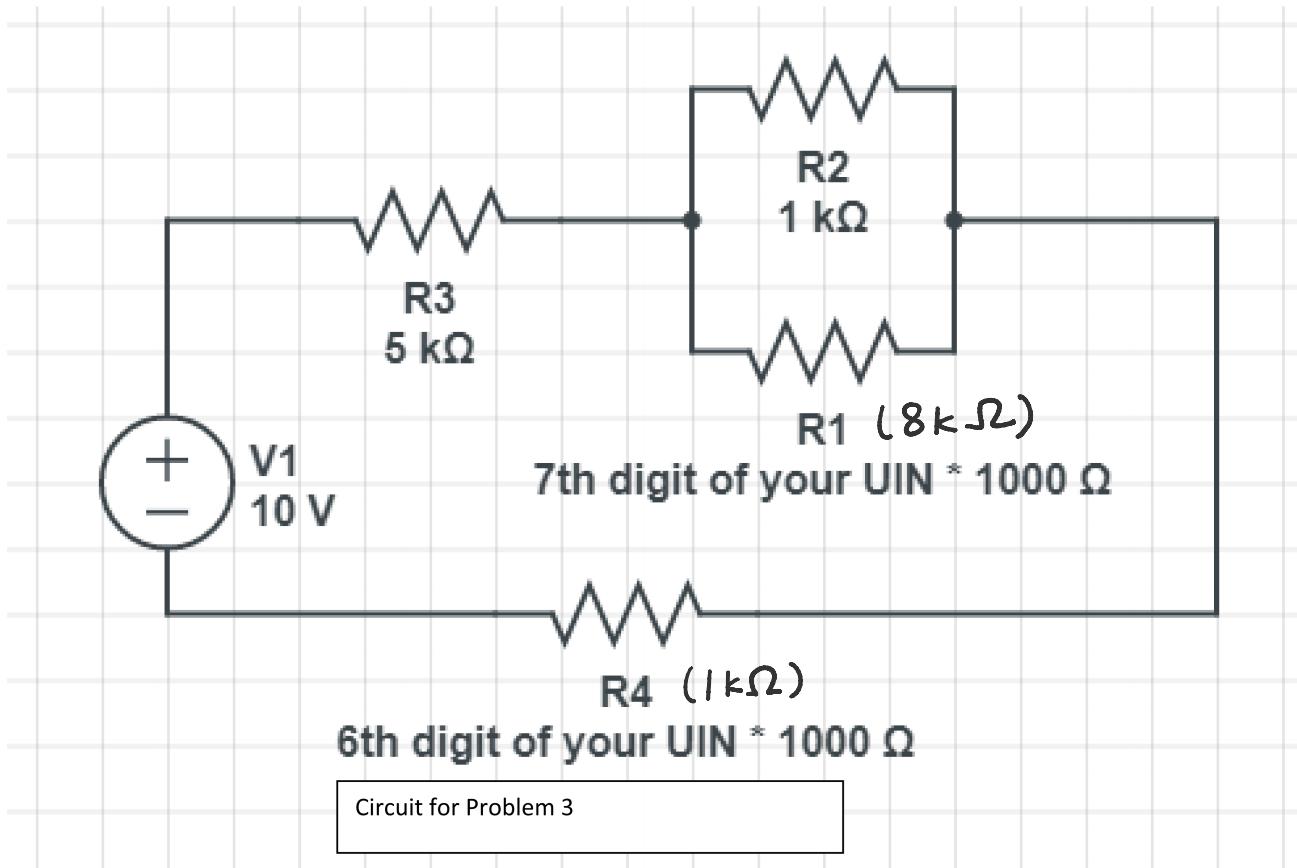Problem 3: Calculate the following values:



The total resistance in the circuit, R_t

$$6.889 \text{ k}\Omega$$

Calculate the voltage across R₁

$$1.26 \text{ volts.}$$

Calculate the current through R₁

$$1.575 \times 10^{-4} \text{ amp.}$$

Calculate the voltage across R₂

$$1.26 \text{ volts.}$$

Calculate the current through R₂

$$1.26 \times 10^{-3} \text{ amp.}$$

Calculate the voltage across R₃

$$7.26 \text{ volts}$$

Calculate the current through R₃

$$1.452 \times 10^{-3} \text{ amp.}$$

Calculate the voltage across R₄

$$1.45 \text{ volts.}$$

Calculate the current through R₄

$$1.452 \times 10^{-3} \text{ amp.}$$

Use this space to show your work for Problem 3.

$$R_T = 5 + \frac{1}{\frac{1}{1} + \frac{1}{8}} + 1 = 5 + \frac{8}{9} + 1 = 6.889 \text{ k}\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{10 \text{ V}}{6.889 \text{ k}\Omega} = 1.452 \times 10^{-3} \text{ amp.}$$

$$\text{So, } I_3 = I_4 = 1.452 \times 10^{-3} \text{ amp.}$$

$$\Rightarrow V_3 = (5 \times 10^3)(1.452 \times 10^{-3}) \text{ volt}$$

$$= 7.26 \text{ volts.}$$

$$V_4 = (1 \times 10^3)(1.452 \times 10^{-3}) \text{ volt.}$$

$$= 1.452 \text{ volts.}$$

$$\text{So, } V_1 = V_2 = 10 - (7.26 + 1.45)$$

$$= 1.26 \text{ volts.}$$

$$I_1 = \frac{1.26 \text{ V}}{8 \times 10^3 \Omega} = 1.575 \times 10^{-4} \text{ amp.}$$

$$I_2 = \frac{1.26 \text{ V}}{1 \times 10^{-3} \Omega} = 1.26 \times 10^{-3} \text{ amp.}$$